

18-447

# Computer Architecture

## Lecture 5: Intro to Microarchitecture: Single-Cycle

Prof. Onur Mutlu

Carnegie Mellon University

Spring 2015, 1/26/2015

# Agenda for Today & Next Few Lectures

---

- Start Microarchitecture
- Single-cycle Microarchitectures
- Multi-cycle Microarchitectures
- Microprogrammed Microarchitectures
- Pipelining
- Issues in Pipelining: Control & Data Dependence Handling, State Maintenance and Recovery, ...

# Recap of Two Weeks and Last Lecture

---

- Computer Architecture Today and Basics (Lectures 1 & 2)
- Fundamental Concepts (Lecture 3)
- ISA basics and tradeoffs (Lectures 3 & 4)
  
- Last Lecture: ISA tradeoffs continued + MIPS ISA
  - Instruction length
  - Uniform vs. non-uniform decode
  - Number of registers
  - Addressing modes
  - Aligned vs. unaligned access
  - RISC vs. CISC properties
  - MIPS ISA Overview

# Assignment for You

---

- Not to be turned in
- As you learn the MIPS ISA, think about what tradeoffs the designers have made
  - in terms of the ISA properties we talked about
- And, think about the pros and cons of design choices
  - In comparison to ARM, Alpha
  - In comparison to x86, VAX
- And, think about the potential mistakes
  - Branch delay slot?
  - Load delay slot?
  - No FP, no multiply, MIPS (initial)

**Look Backward**

**Microprocessor without Interlocked Pipelined Stages**

The hardware doesn't do anything to detect the dependency between instructions, everything is handled by the software, so that you can design a microprocessor that is simple

# Food for Thought for You

---

- How would you design a new ISA?
- Where would you place it?
- What design choices would you make in terms of ISA properties?
- What would be the first question you ask in this process?
  - “What is my **design point**?”

**Look Forward & Up**

# Review: Other Example ISA-level Tradeoffs

---

- Condition codes vs. not
- VLIW vs. single instruction
- SIMD (single instruction multiple data) vs. SISD
- Precise vs. imprecise exceptions
- Virtual memory vs. not
- Unaligned access vs. not
- Hardware interlocks vs. software-guaranteed interlocking
- Software vs. hardware managed page fault handling
- Cache coherence (hardware vs. software)
- ...

**Think Programmer vs. (Micro)architect**

---

# Review: A Note on RISC vs. CISC

---

- Usually, ...
  - RISC
    - ❑ Simple instructions
    - ❑ Fixed length
    - ❑ Uniform decode
    - ❑ Few addressing modes
  - CISC
    - ❑ Complex instructions
    - ❑ Variable length
    - ❑ Non-uniform decode
    - ❑ Many addressing modes
- Power

# Now That We Have an ISA

---

- How do we implement it?
- i.e., how do we design a system that obeys the hardware/software interface?
- Aside: “System” can be solely hardware or a combination of hardware and software
  - Remember “Translation of ISAs”
  - A virtual ISA can be converted by “software” into an implementation ISA
- We will assume “hardware” for most lectures




# Implementing the ISA: Microarchitecture Basics

# How Does a Machine Process Instructions?


---

- What does processing an instruction mean?
- Remember the von Neumann model

 AS = Architectural (programmer visible) state before an instruction is processed



 Process instruction The programmer see nothing intermediate



AS' = Architectural (programmer visible) state after an instruction is processed

- Processing an instruction: Transforming AS to AS' according to the ISA specification of the instruction

# The “Process instruction” Step

---


- ISA specifies abstractly what  $AS'$  should be, given an instruction and  $AS$ 
  - It defines an abstract finite state machine where
    - State = programmer-visible state
    - Next-state logic = instruction execution specification
  - From ISA point of view, there are no “intermediate states” between  $AS$  and  $AS'$  during instruction execution
    - One state transition per instruction
- Microarchitecture implements how  $AS$  is transformed to  $AS'$ 
  - There are many choices in implementation
  - We can have programmer-invisible state to optimize the speed of instruction execution: multiple state transitions per instruction
    - Choice 1:  $AS \rightarrow AS'$  (transform  $AS$  to  $AS'$  in a single clock cycle)
    - Choice 2:  $AS \rightarrow AS+MS1 \rightarrow AS+MS2 \rightarrow AS+MS3 \rightarrow AS'$  (take multiple clock cycles to transform  $AS$  to  $AS'$ )  
Microarchitecture State

# A Very Basic Instruction Processing Engine


---

- Each instruction takes a single clock cycle to execute
- Only combinational logic is used to implement instruction execution
  - *No intermediate, programmer-invisible state updates*

 AS = Architectural (programmer visible) state  
at the beginning of a clock cycle



Process instruction in one clock cycle

 


AS' = Architectural (programmer visible) state  
at the end of a clock cycle

# A Very Basic Instruction Processing Engine

---


- Single-cycle machine

 

- What is the *clock cycle time* determined by?
- What is the *critical path* of the combinational logic determined by? The longest instruction to process

# Remember: Programmer Visible (Architectural) State

---

 


Memory  
array of storage locations  
indexed by an address



Registers

 - given special names in the ISA (as opposed to addresses)
- general vs. special purpose



memory address  
of the current instruction

Instructions (and programs) specify how to transform  
the values of programmer visible state

# Single-cycle vs. Multi-cycle Machines

---

## ■ Single-cycle machines

- ❑ Each instruction takes a single clock cycle
- ❑ All state updates made at the end of an instruction's execution
- ❑ Big disadvantage: The slowest instruction determines cycle time → long clock cycle time

## ■ Multi-cycle machines

- ❑ Instruction processing broken into multiple cycles/stages
- ❑ State updates can be made during an instruction's execution
- ❑ Architectural state updates made only at the end of an instruction's execution
- ❑ Advantage over single-cycle: The slowest "stage" determines cycle time

- Both single-cycle and multi-cycle machines literally follow the von Neumann model at the microarchitecture level

# Instruction Processing “Cycle”

---

- Instructions are processed under the direction of a “control unit” step by step.
- Instruction cycle: Sequence of steps to process an instruction
- Fundamentally, there are six phases:
  - Fetch
  - Decode
  - Evaluate Address
  - Fetch Operands
  - Execute
  - Store Result
- Not all instructions require all six stages (see P&P Ch. 4)



# Instruction Processing “Cycle” vs. Machine Clock Cycle

---

- Single-cycle machine:
  - All six phases of the instruction processing cycle take a *single machine clock cycle* to complete
- Multi-cycle machine:
  - All six phases of the instruction processing cycle can take *multiple machine clock cycles* to complete
  - In fact, **each phase can take multiple clock cycles to complete**

# Instruction Processing Viewed Another Way

---

- Instructions transform Data (AS) to Data' (AS')
- This transformation is done by functional units
  - Units that “operate” on data
- These units need to be told what to do to the data
- An instruction processing engine consists of two components
  - **Datapath**: Consists of hardware elements that deal with and transform data signals
    - functional units that operate on data
    - hardware structures (e.g. wires and muxes) that enable the flow of data into the functional units and registers
    - storage units that store data (e.g., registers)
  - **Control logic**: Consists of hardware elements that determine control signals, i.e., signals that specify what the datapath elements should do to the data

# Single-cycle vs. Multi-cycle: Control & Data

---

- Single-cycle machine:
  - Control signals are generated in the same clock cycle as the one during which data signals are operated on
  - Everything related to an instruction happens in one clock cycle (serialized processing)
- Multi-cycle machine:
  - Control signals needed in the next cycle can be generated in the current cycle
  - Latency of control processing can be overlapped with latency of datapath operation (more parallelism)
- We will see the difference clearly in *microprogrammed multi-cycle microarchitectures*

# Many Ways of Datapath and Control Design

---

- There are many ways of designing the data path and control logic
- Single-cycle, multi-cycle, pipelined datapath and control
- Single-bus vs. multi-bus datapaths
  - See your homework 2 question
- Hardwired/combinational vs. microcoded/microprogrammed control
  - Control signals generated by combinational logic versus
  - Control signals stored in a **memory structure**
    - Can be update (when there is a bug in ISA)
- Control signals and structure depend on the datapath design

# Flash-Forward: Performance Analysis

---

- Execution time of an instruction

Cycle per instruction

- $\{\text{CPI}\} \times \{\text{clock cycle time}\}$

- Execution time of a program

- Sum over all instructions  $[\{\text{CPI}\} \times \{\text{clock cycle time}\}]$

- $\{\# \text{ of instructions}\} \times \{\text{Average CPI}\} \times \{\text{clock cycle time}\}$

- Single cycle microarchitecture performance

- $\text{CPI} = 1$

- $\text{Clock cycle time} = \text{long}$

- Multi-cycle microarchitecture performance

- $\text{CPI} = \text{different for each instruction}$

- $\text{Average CPI} \rightarrow \text{hopefully small}$

- $\text{Clock cycle time} = \text{short}$

**Now, we have  
two degrees of freedom  
to optimize independently**


# A Single-Cycle Microarchitecture

## *A Closer Look*

# Remember...


---

- Single-cycle machine

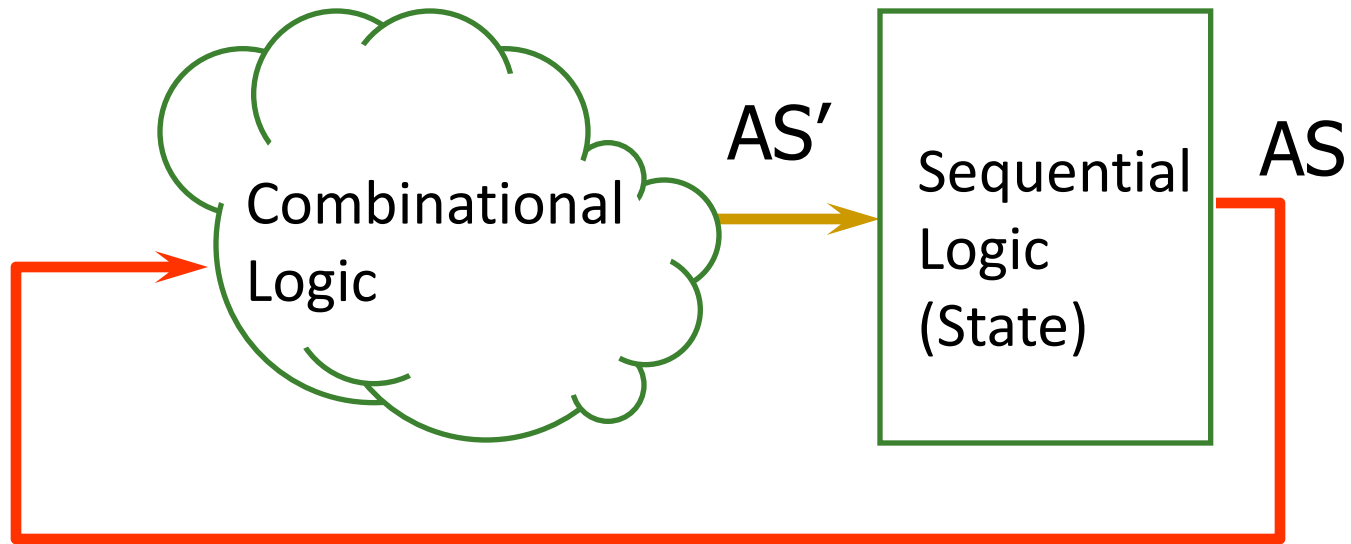

# Let's Start with the State Elements

## ■ Data and control inputs

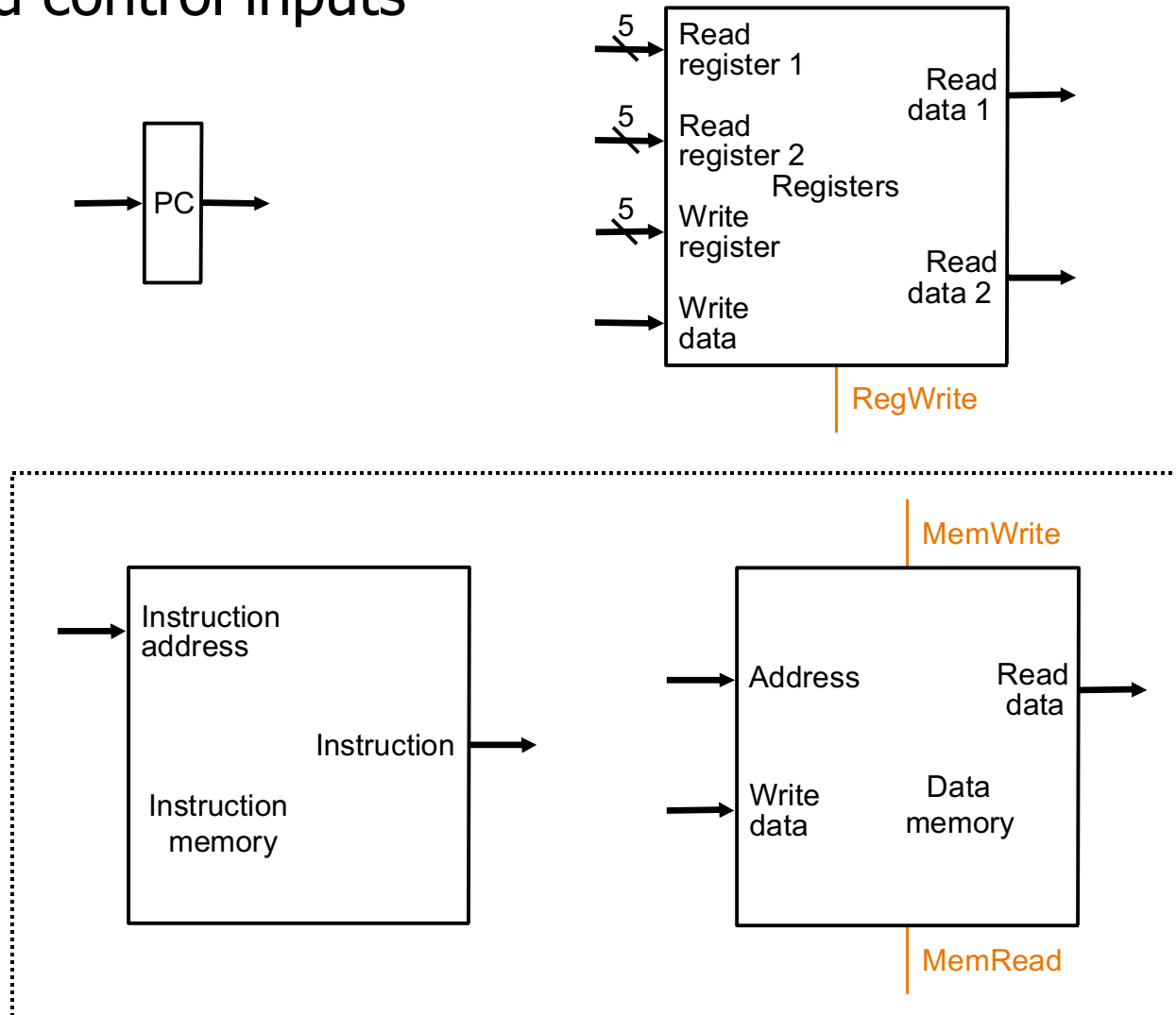




# For Now, We Will Assume

---


- “Magic” memory and register file
- Combinational read
  - output of the read data port is a combinational function of the register file contents and the corresponding read select port
- Synchronous write
  - the selected register is updated on the positive edge clock transition when write enable is asserted
    - Cannot affect read output in between clock edges
- Single-cycle, synchronous memory
  - Contrast this with memory that tells when the data is ready
  - i.e., Ready bit: indicating the read or write is done
 
# Instruction Processing

- 5 generic steps (P&H book)
  - ❑ Instruction fetch (IF)
  - ❑ Instruction decode and register operand fetch (ID/RF)
  - ❑ Execute/Evaluate memory address (EX/AG)
  - ❑ Memory operand fetch (MEM)
  - ❑ Store/writeback result (WB)


 
# What Is To Come: The Full MIPS Datapath



\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier.  
ALL RIGHTS RESERVED.]

# Single-Cycle Datapath for *Arithmetic and Logical Instructions*


# R-Type ALU Instructions

---

- Assembly (e.g., register-register signed addition)

ADD  $rd_{reg}$   $rs_{reg}$   $rt_{reg}$


- Machine encoding

 

- Semantics

if MEM[PC] == ADD rd rs rt  
     $GPR[rd] \leftarrow GPR[rs] + GPR[rt]$   
     $PC \leftarrow PC + 4$

# ALU Datapath

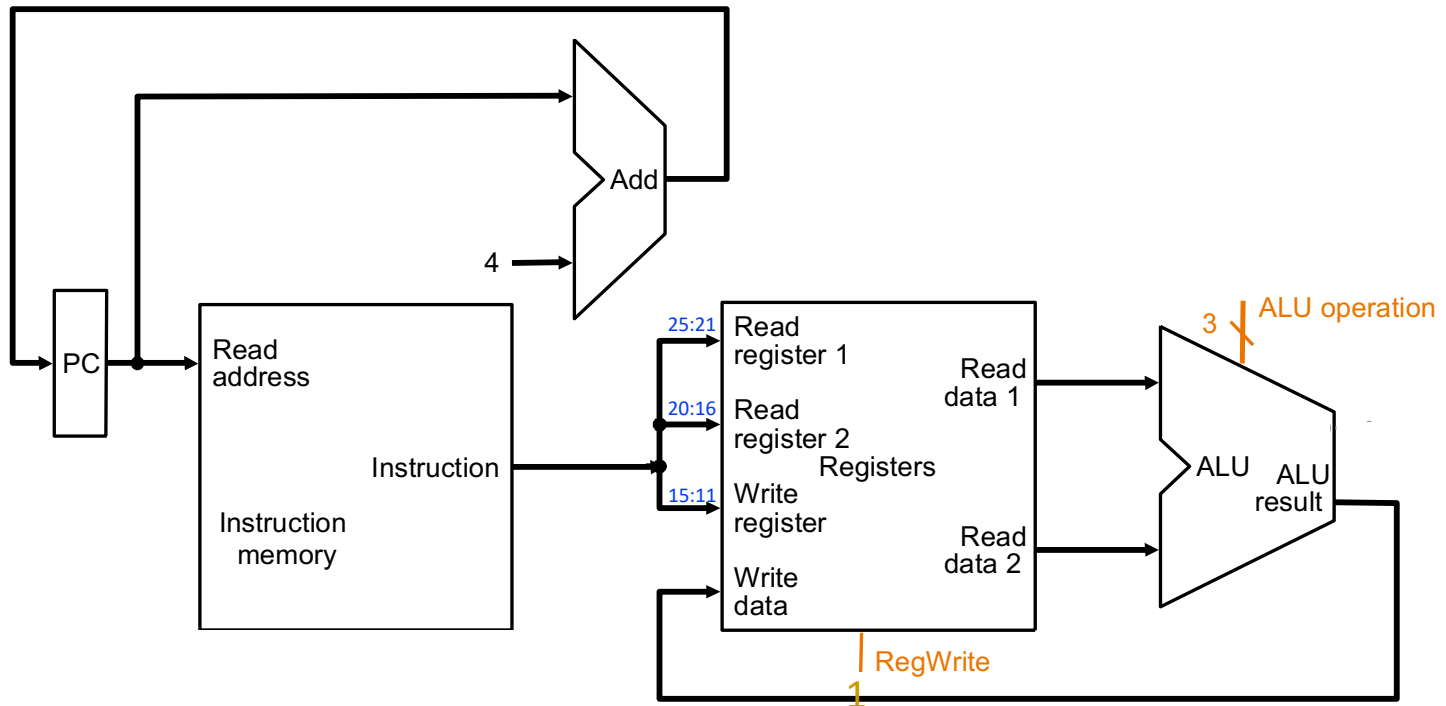

if MEM[PC] == ADD rd rs rt  
GPR[rd]  $\leftarrow$  GPR[rs] + GPR[rt]  
PC  $\leftarrow$  PC + 4



IF	ID	EX	MEM	WB
----	----	----	-----	----

Combinational  
state update logic


# I-Type ALU Instructions

---

- Assembly (e.g., register-immediate signed additions)

ADDI  $rt_{reg}$   $rs_{reg}$   $immediate_{16}$

- Machine encoding

 

I-type


- Semantics

if  $MEM[PC] == \text{ADDI } rt \text{ } rs \text{ } immediate$

$GPR[rt] \leftarrow GPR[rs] + \text{sign-extend}(immediate)$

$PC \leftarrow PC + 4$

# Datapath for R and I-Type ALU Insts.

 

if MEM[PC] == ADDI rt rs immediate  
 $GPR[rt] \leftarrow GPR[rs] + \text{sign-extend}(\text{immediate})$   
 $PC \leftarrow PC + 4$



Combinational  
state update logic



# Single-Cycle Datapath for *Data Movement Instructions*


# Load Instructions

---

- Assembly (e.g., load 4-byte word)

LW  $rt_{reg}$   $offset_{16}$  ( $base_{reg}$ )

- Machine encoding

 

I-type

- Semantics


if  $MEM[PC] == LW \ rt \ offset_{16} \ (base)$

$EA = \text{sign-extend}(offset) + GPR[base]$

$GPR[rt] \leftarrow MEM[ \text{translate}(EA) ]$

$PC \leftarrow PC + 4$

# LW Datapath

 

if  $\text{MEM}[\text{PC}] == \text{LW rt offset}_{16} (\text{base})$   
 $\text{EA} = \text{sign-extend}(\text{offset}) + \text{GPR}[\text{base}]$   
 $\text{GPR}[\text{rt}] \leftarrow \text{MEM}[\text{translate}(\text{EA})]$   
 $\text{PC} \leftarrow \text{PC} + 4$

IF	ID	EX	MEM	WB
----	----	----	-----	----

Combinational  
state update logic


# Store Instructions

---

- Assembly (e.g., store 4-byte word)

$\text{SW } \text{rt}_{\text{reg}} \text{ offset}_{16} (\text{base}_{\text{reg}})$

- Machine encoding

 

I-type

- Semantics


if  $\text{MEM}[\text{PC}] == \text{SW } \text{rt } \text{offset}_{16} (\text{base})$

$\text{EA} = \text{sign-extend}(\text{offset}) + \text{GPR}[\text{base}]$

$\text{MEM}[\text{translate}(\text{EA})] \leftarrow \text{GPR}[\text{rt}]$

$\text{PC} \leftarrow \text{PC} + 4$

# SW Datapath

 


if  $\text{MEM}[\text{PC}] == \text{SW rt offset}_{16}(\text{base})$   
 $\text{EA} = \text{sign-extend}(\text{offset}) + \text{GPR}[\text{base}]$   
 $\text{MEM}[\text{translate}(\text{EA})] \leftarrow \text{GPR}[\text{rt}]$   
 $\text{PC} \leftarrow \text{PC} + 4$


IF	ID	EX	MEM	WB
----	----	----	-----	----

Combinational  
state update logic

# Load-Store Datapath

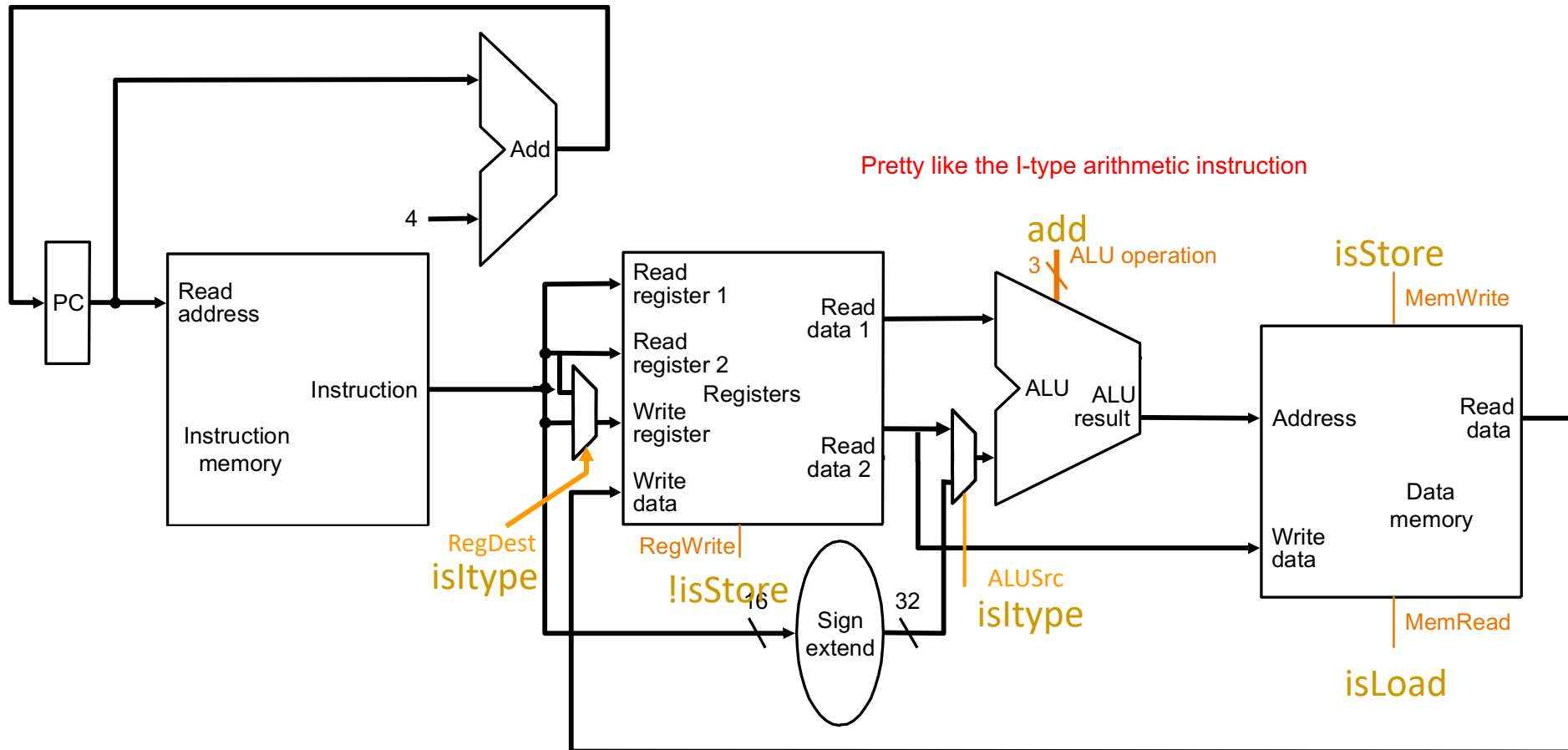

# Datapath for Non-Control-Flow Insts.

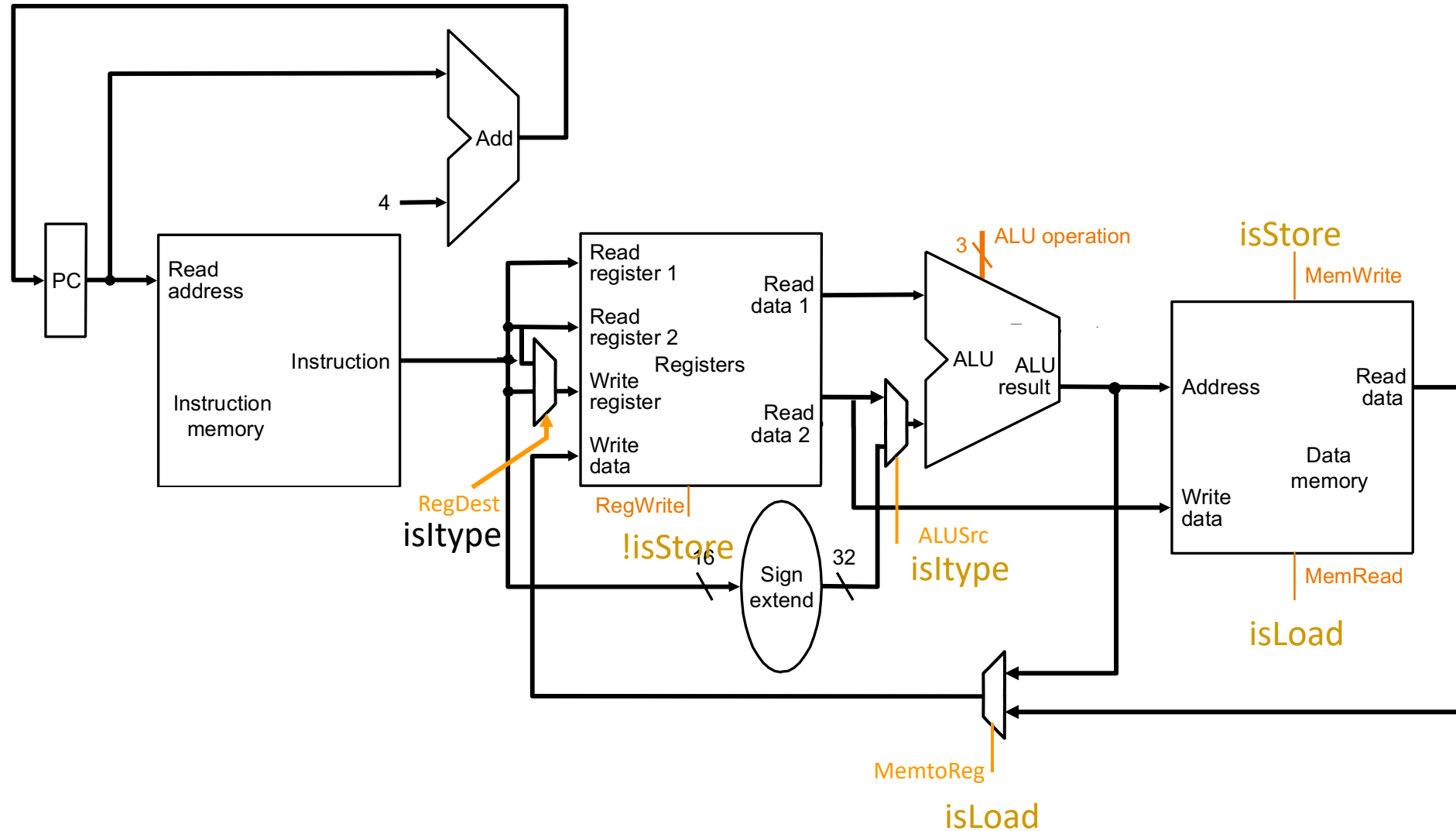

# Single-Cycle Datapath for *Control Flow Instructions*




# Unconditional Jump Instructions

---

- Assembly

J immediate<sub>26</sub>

- Machine encoding

 

J-type


- Semantics

if MEM[PC] == J immediate<sub>26</sub>

target = { PC[31:28], immediate<sub>26</sub>, 2' b00 }

PC ← target

# Unconditional Jump Datapath

 

\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

if MEM[PC]==J immediate26  
 PC = { PC[31:28], immediate26, 2' b00 }

What about JR, JAL, JALR?

# Aside: MIPS Cheat Sheet

---

- [http://www.ece.cmu.edu/~ece447/s15/lib/exe/fetch.php?media=mips\\_reference\\_data.pdf](http://www.ece.cmu.edu/~ece447/s15/lib/exe/fetch.php?media=mips_reference_data.pdf)
- On the 447 website


# Conditional Branch Instructions

---

- Assembly (e.g., branch if equal)

BEQ  $rs_{reg}$   $rt_{reg}$   $immediate_{16}$

- Machine encoding

 

I-type

- Semantics (assuming no branch delay slot)


if  $MEM[PC] == BEQ\ rs\ rt\ immediate_{16}$

target =  $PC + 4 + \text{sign-extend}(immediate) \times 4$

if  $GPR[rs] == GPR[rt]$  then  $PC \leftarrow \text{target}$


else  $PC \leftarrow PC + 4$
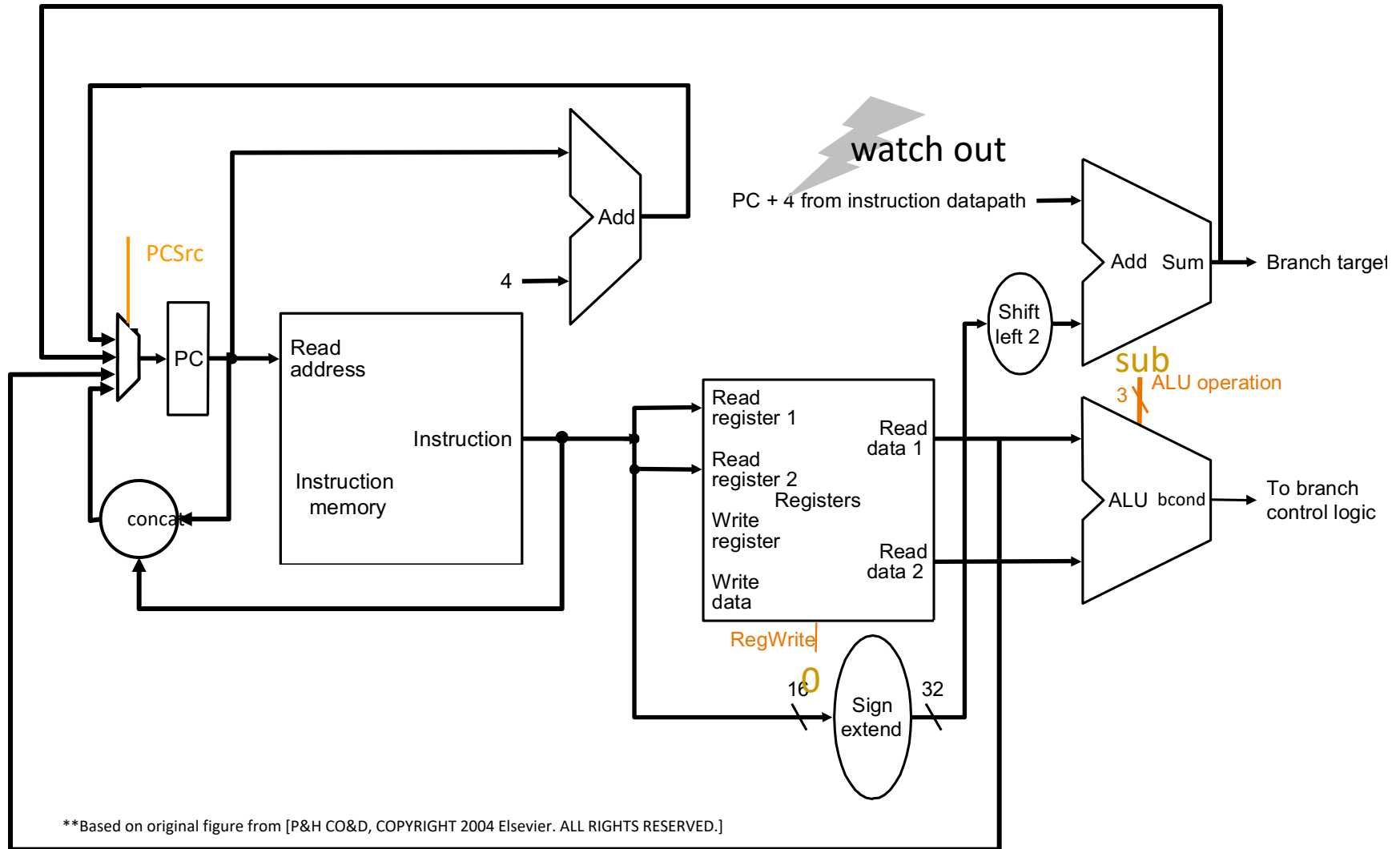
# Conditional Branch Datapath (for you to finish)



How to uphold the delayed branch semantics?


# Putting It All Together

 

# Single-Cycle Control Logic
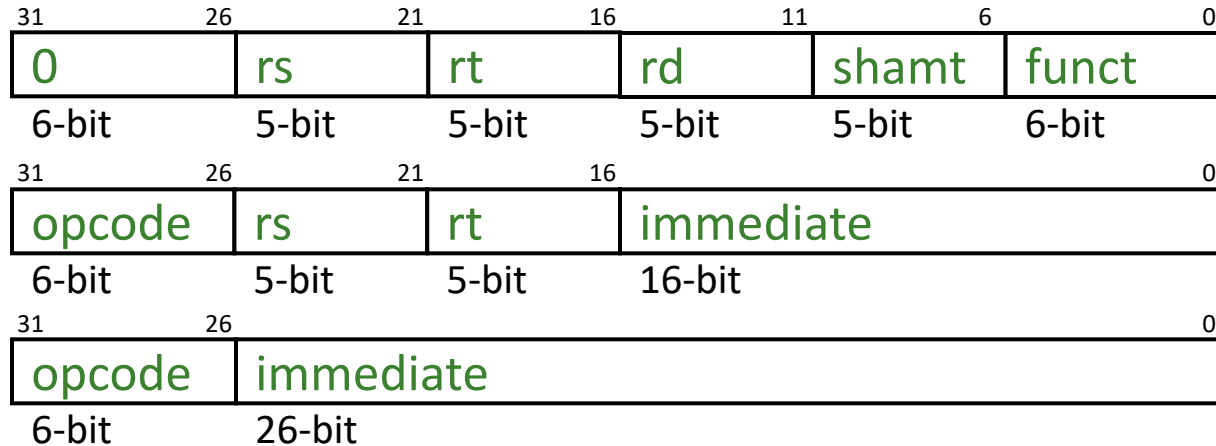
# Single-Cycle Hardwired Control

- As combinational function of  $\text{Inst} = \text{MEM}[\text{PC}]$



R-type

I-type

J-type

- Consider
  - All R-type and I-type ALU instructions
  - LW and SW
  - BEQ, BNE, BLEZ, BGTZ
  - J, JR, JAL, JALR



# Single-Bit Control Signals

---

	When De-asserted	When asserted	Equation
RegDest	GPR write select according to <b>rt</b> , i.e., inst[20:16]	GPR write select according to <b>rd</b> , i.e., inst[15:11]	<b>opcode</b> ==0
ALUSrc	2 <sup>nd</sup> ALU input from 2 <sup>nd</sup> GPR read port	2 <sup>nd</sup> ALU input from sign-extended 16-bit immediate	( <b>opcode</b> !=0) && ( <b>opcode</b> !=BEQ) && ( <b>opcode</b> !=BNE)
MemtoReg	Steer ALU result to GPR write port	steer memory load to GPR wr. port	<b>opcode</b> ==LW
RegWrite	GPR write disabled	GPR write enabled	( <b>opcode</b> !=SW) && ( <b>opcode</b> !=Bxx) && ( <b>opcode</b> !=J) && ( <b>opcode</b> !=JR))

# Single-Bit Control Signals

---

	When De-asserted	When asserted	Equation
MemRead	Memory read disabled	Memory read port return load value	<code>opcode==LW</code>
MemWrite	Memory write disabled	Memory write enabled	<code>opcode==SW</code>
PCSrc <sub>1</sub>	According to PCSrc <sub>2</sub>	next PC is based on 26-bit immediate jump target	<code>(opcode==J)    (opcode==JAL)</code>
PCSrc <sub>2</sub>	next PC = PC + 4	next PC is based on 16-bit immediate branch target	<code>(opcode==Bxx) &amp;&amp; "bcond is satisfied"</code>

# ALU Control

---

- case **opcode**

- ‘0’  $\Rightarrow$  select operation according to **funct**

- ‘ALUi’  $\Rightarrow$  selection operation according to **opcode**

- ‘LW’  $\Rightarrow$  select addition

- ‘SW’  $\Rightarrow$  select addition

- ‘Bxx’  $\Rightarrow$  select bcond generation function


- \_\_\_  $\Rightarrow$  don't care

- Example ALU operations

- ❑ ADD, SUB, AND, OR, XOR, NOR, etc.


- ❑ bcond on equal, not equal, LE zero, GT zero, etc.


# R-Type ALU

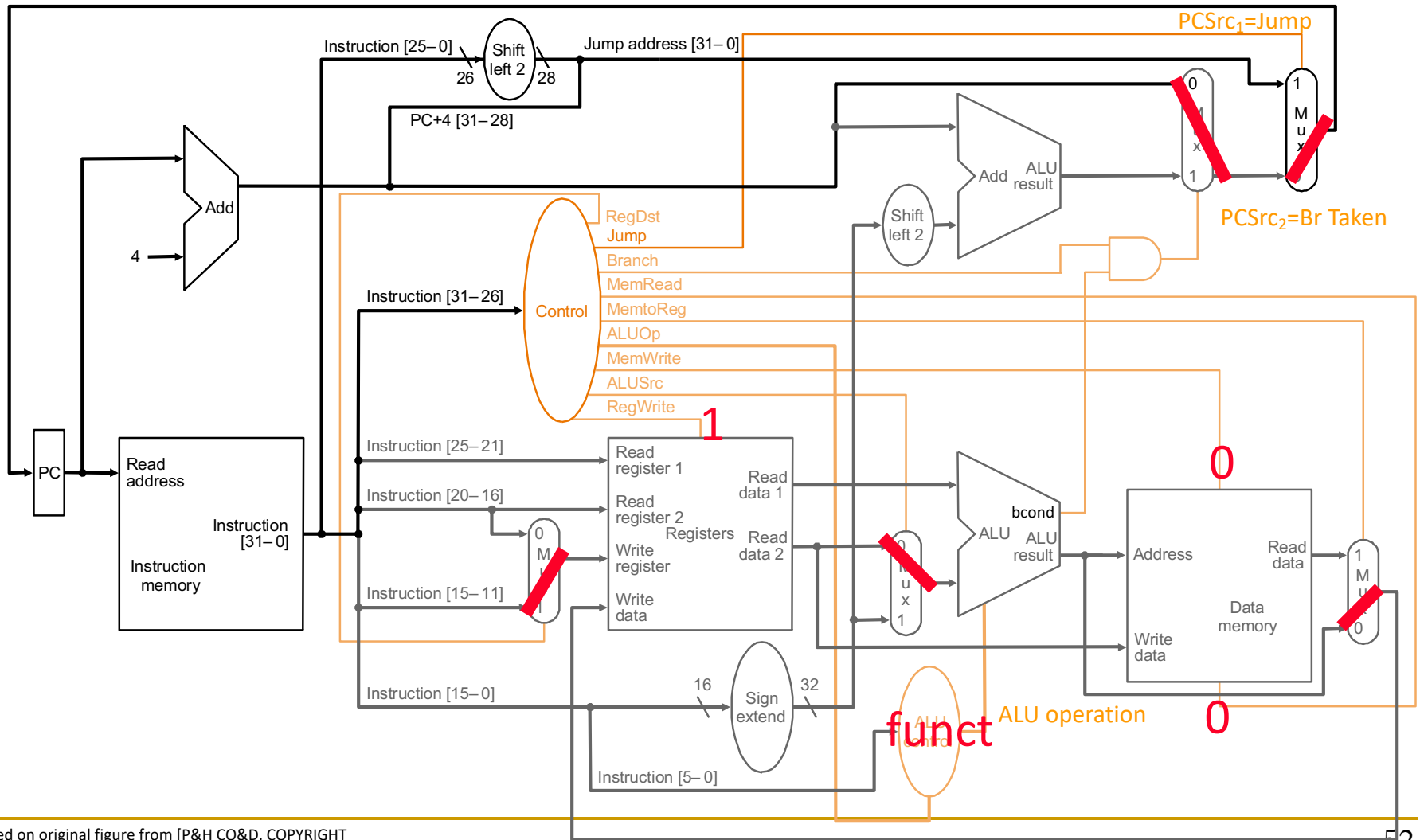


\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

# I-Type ALU

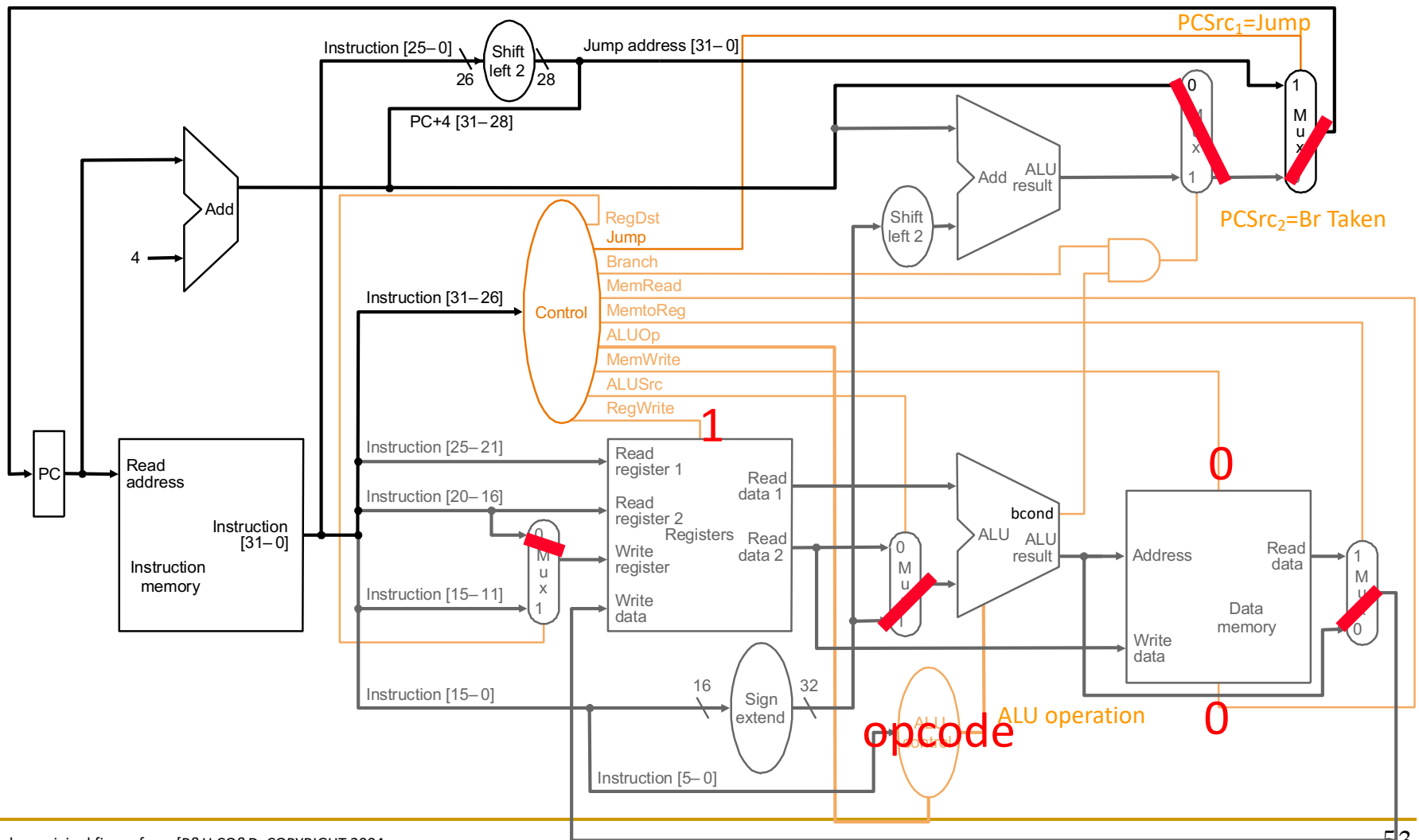


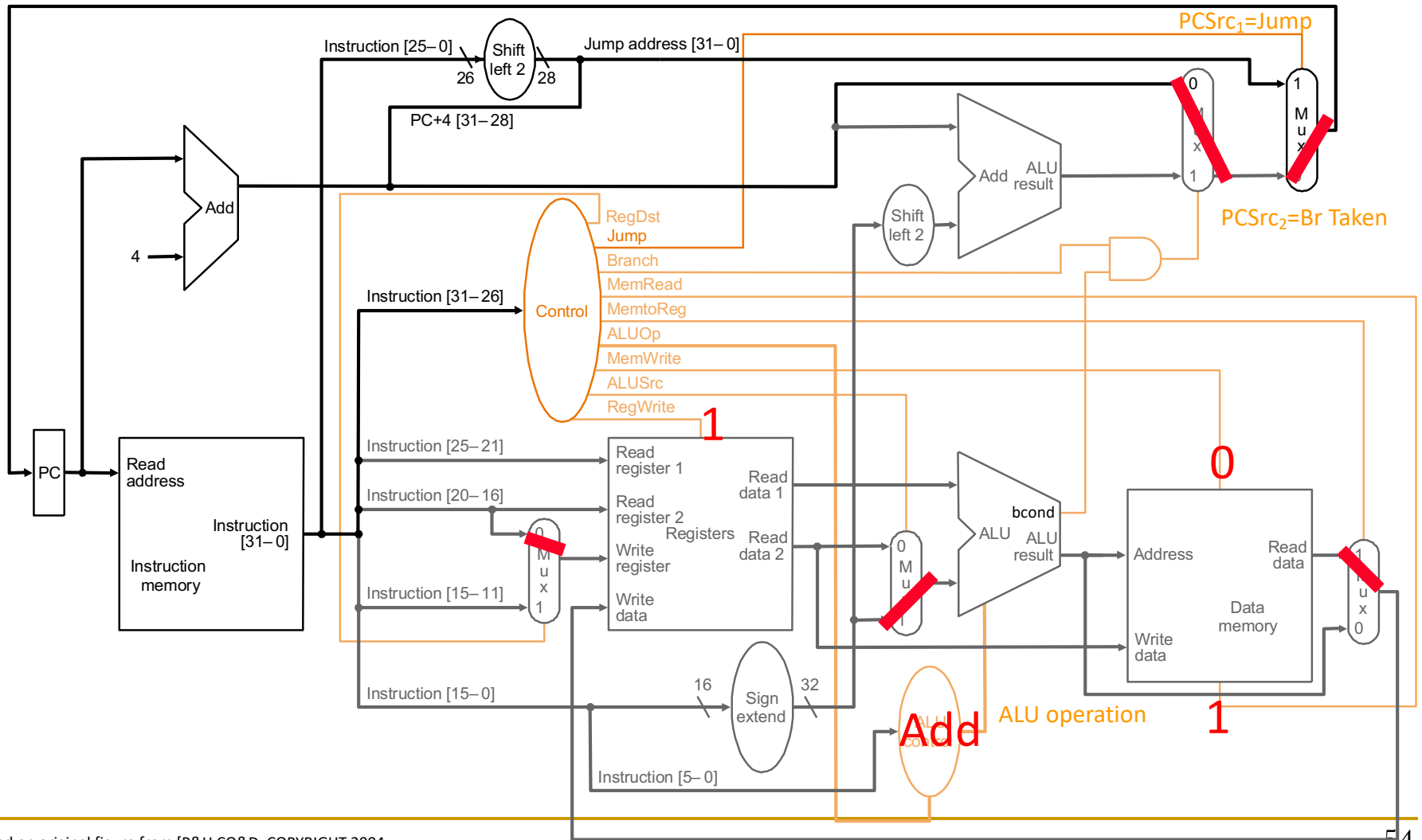

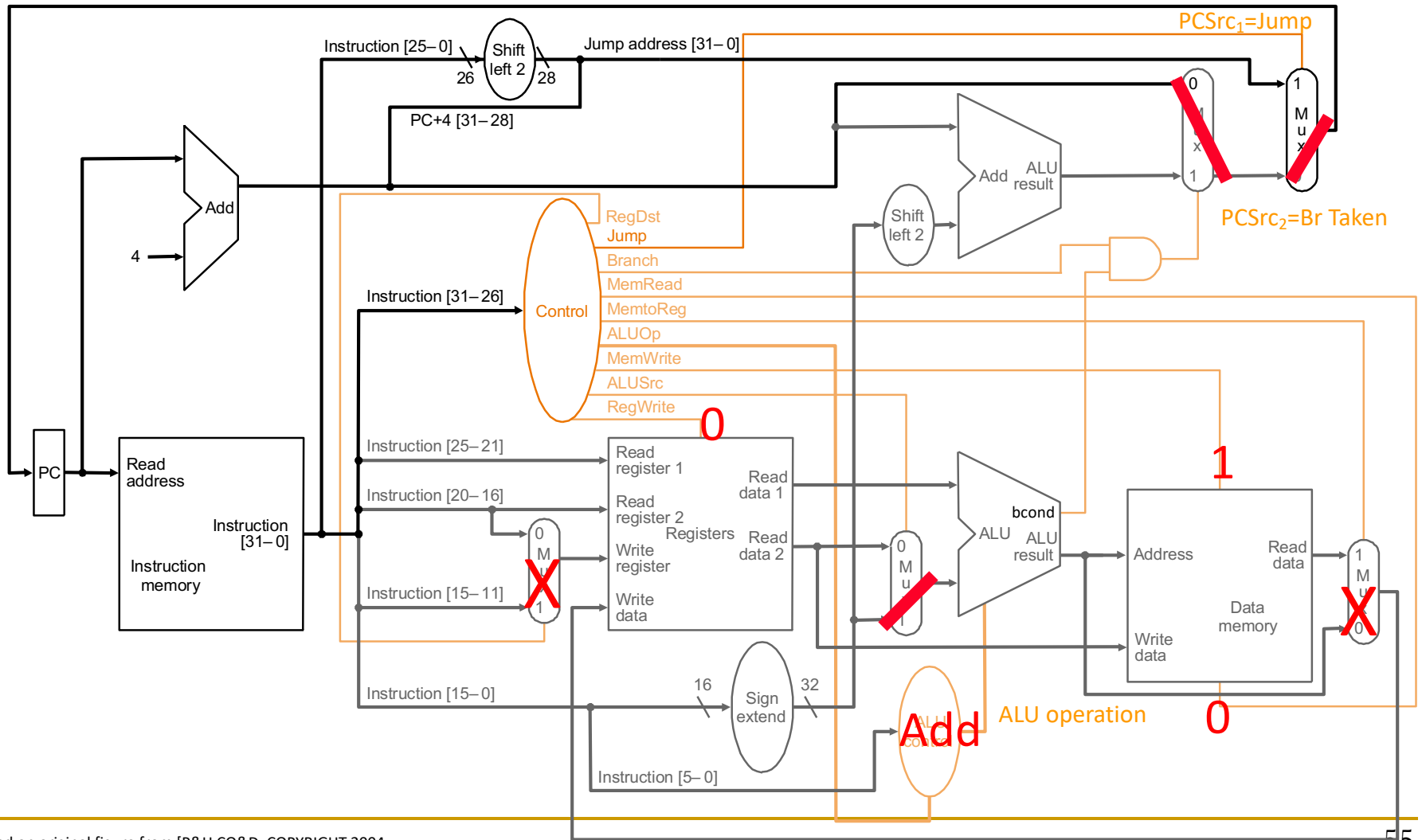
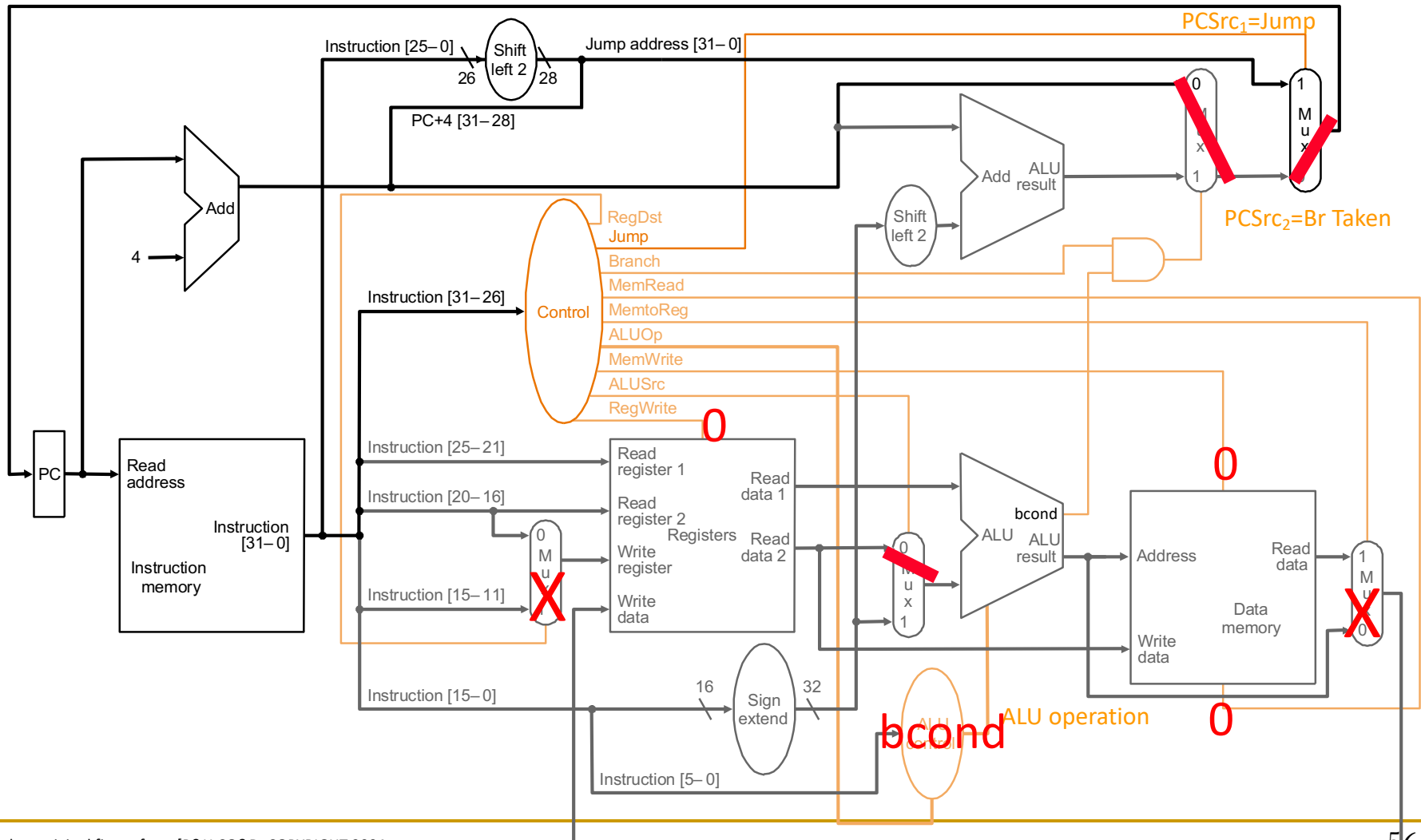
# Branch (Not Taken)


Some control signals are dependent on the processing of data





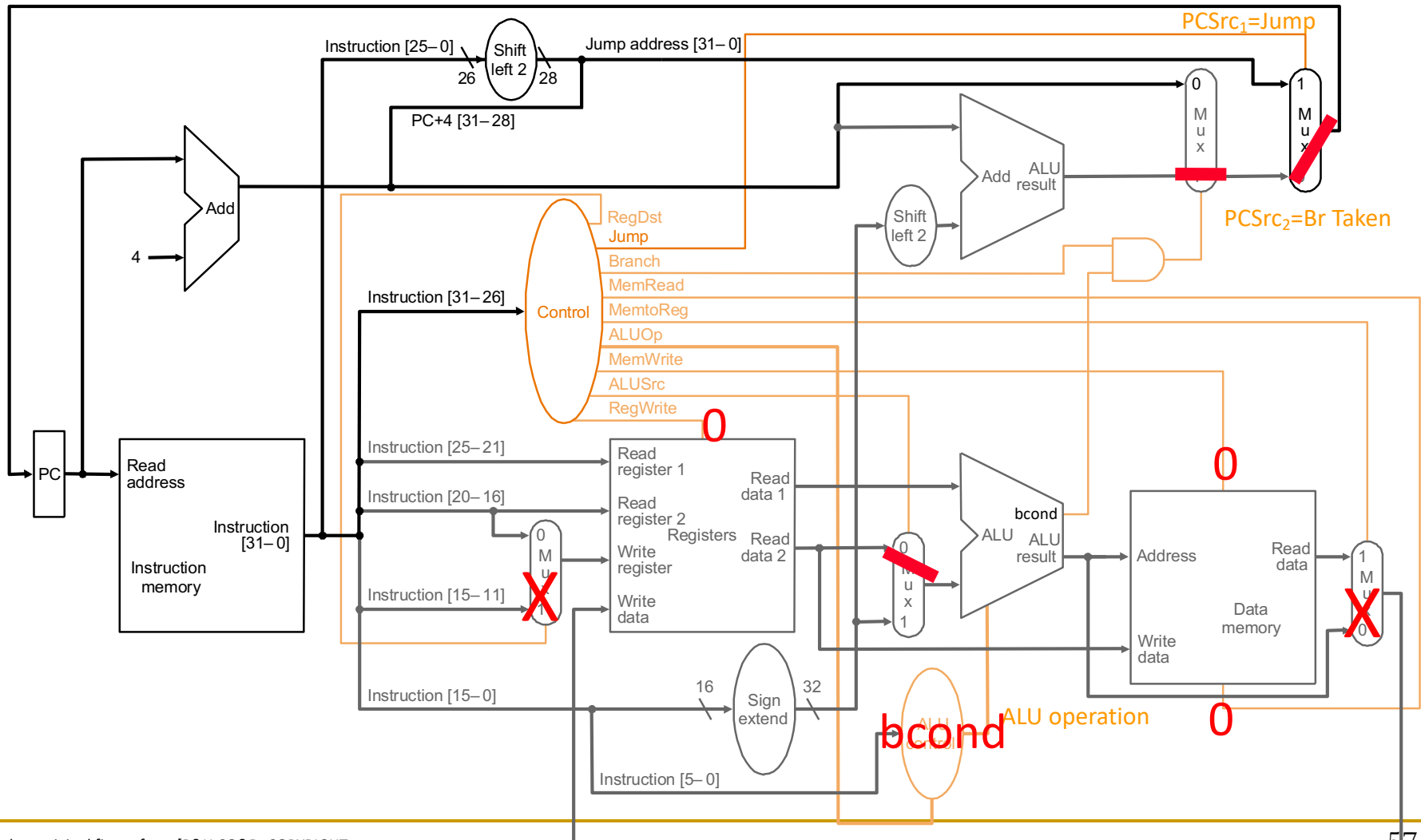
# Branch (Taken)

Some control signals are dependent on the processing of data



# Jump

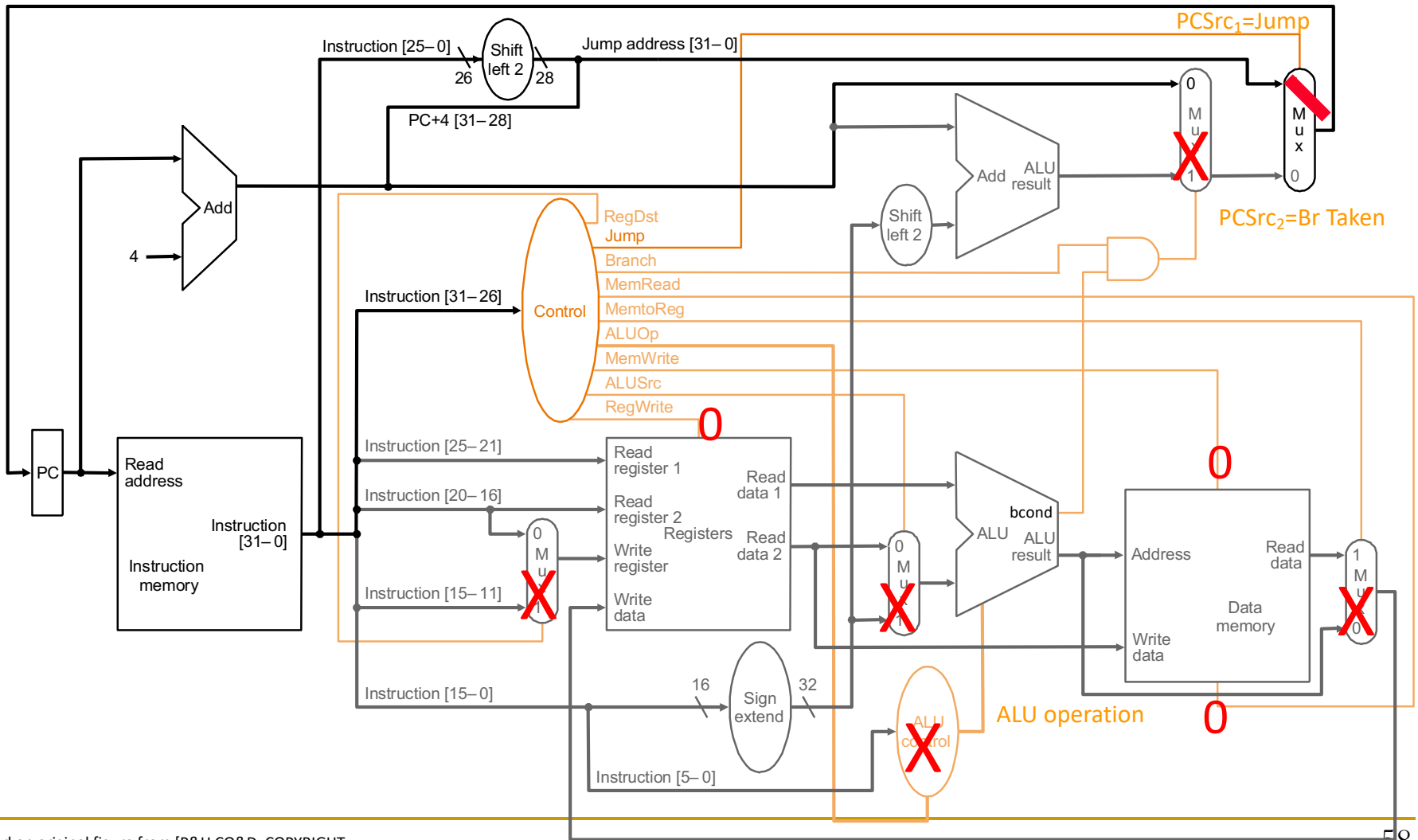

\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

# What is in That Control Box?

---

- Combinational Logic → **Hardwired Control**
  - Idea: Control signals generated combinatorially based on instruction
  - Necessary in a single-cycle microarchitecture...
- Sequential Logic → **Sequential/Microprogrammed Control**
  - Idea: A memory structure contains the control signals associated with an instruction
  - Control Store

# Evaluating the Single-Cycle Microarchitecture

# A Single-Cycle Microarchitecture

---

- Is *this* a good idea/design?
- When is this a good design?
- When is this a bad design?
- How can we design a better microarchitecture?

# A Single-Cycle Microarchitecture: Analysis

---

- Every instruction takes 1 cycle to execute
  - CPI (Cycles per instruction) is strictly 1
- How long each instruction takes is determined by how long the slowest instruction takes to execute
  - Even though many instructions do not need that long to execute
- Clock cycle time of the microarchitecture is determined by how long it takes to complete the slowest instruction
  - Critical path of the design is determined by the processing time of the slowest instruction

# What is the Slowest Instruction to Process?

---

- Let's go back to the basics
  - All six phases of the instruction processing cycle take a *single machine clock cycle* to complete
    - Fetch
    - Decode
    - Evaluate Address
    - Fetch Operands
    - Execute
    - Store Result
1. Instruction fetch (IF)
  2. Instruction decode and register operand fetch (ID/RF)
  3. Execute/Evaluate memory address (EX/AG)
  4. Memory operand fetch (MEM)
  5. Store/writeback result (WB)
- Do each of the above phases take the same time (latency) for all instructions?

# Single-Cycle Datapath Analysis


---

- Assume
  - ❑ memory units (read or write): 200 ps
  - ❑ ALU and adders: 100 ps
  - ❑ register file (read or write): 50 ps
  - ❑ other combinational logic: 0 ps

steps	IF	ID	EX	MEM	WB	Delay
resources	mem	RF	ALU	mem	RF	
R-type	200	50	100		50	400
I-type	200	50	100		50	400
LW	200	50	100	200	50	600
SW	200	50	100	200		550
Branch	200	50	100			350
Jump	200					200




# Let's Find the Critical Path

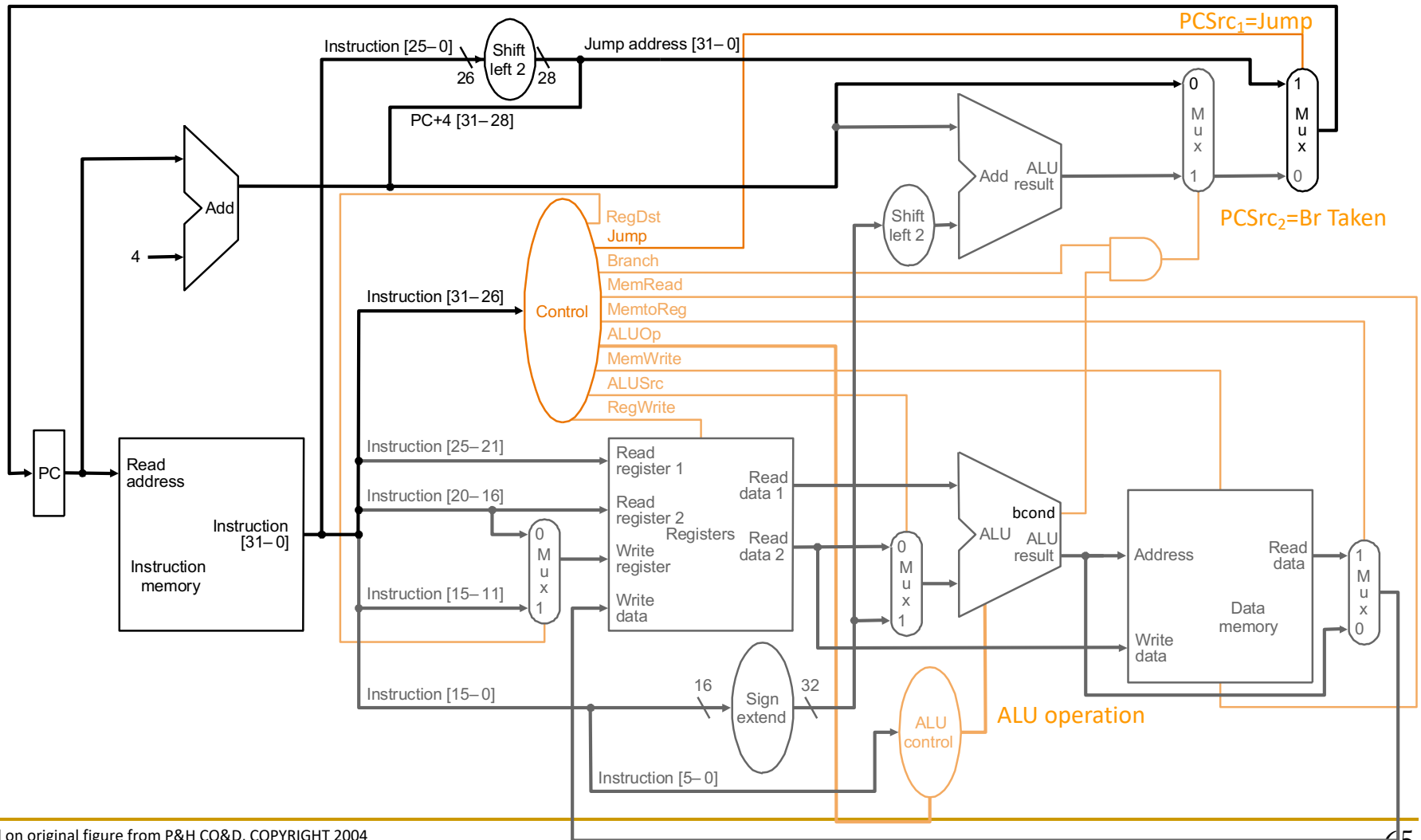


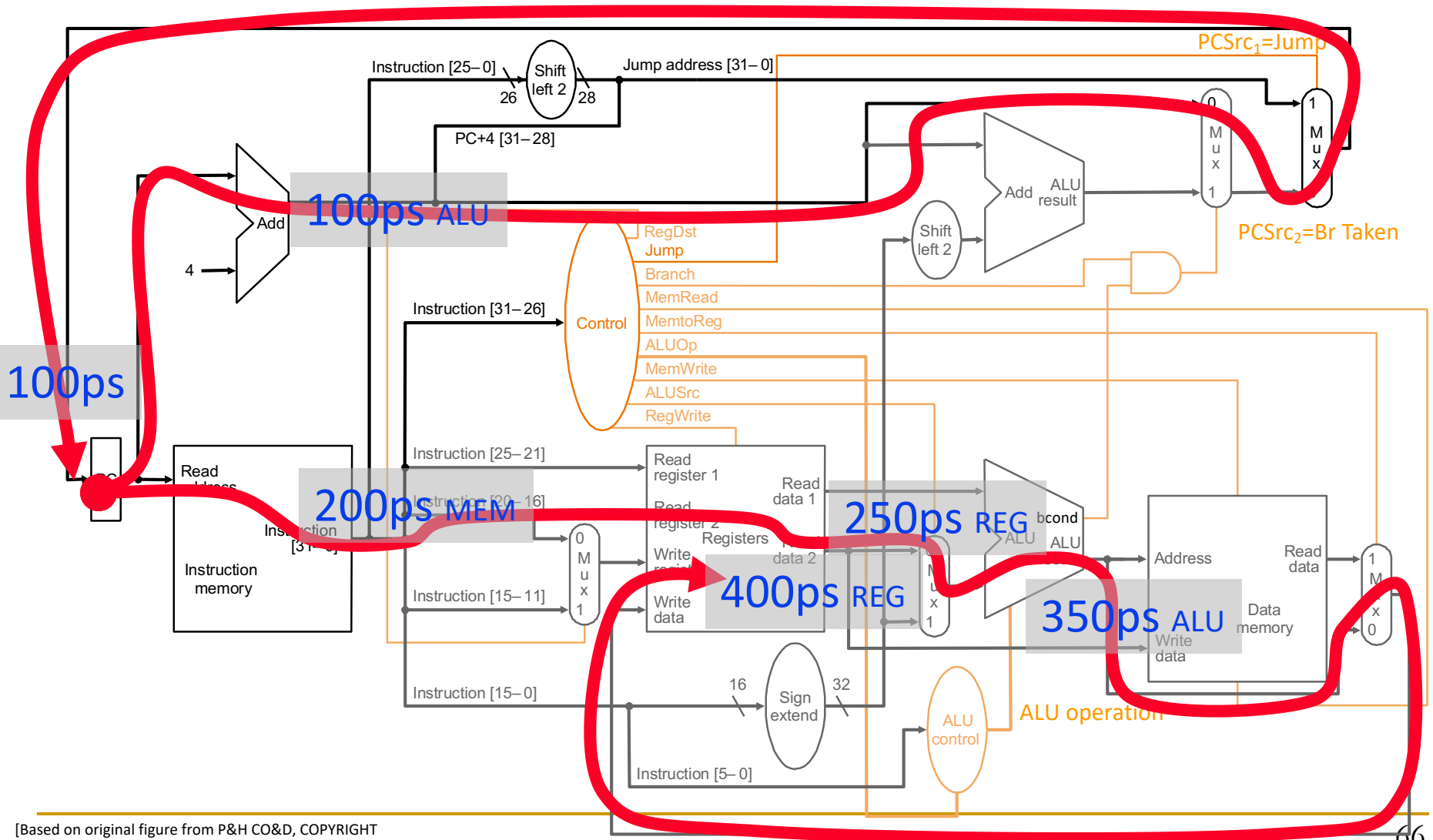
# R-Type and I-Type ALU

Only registers, do not need to access memory when do calculation




 [Based on original figure from P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]



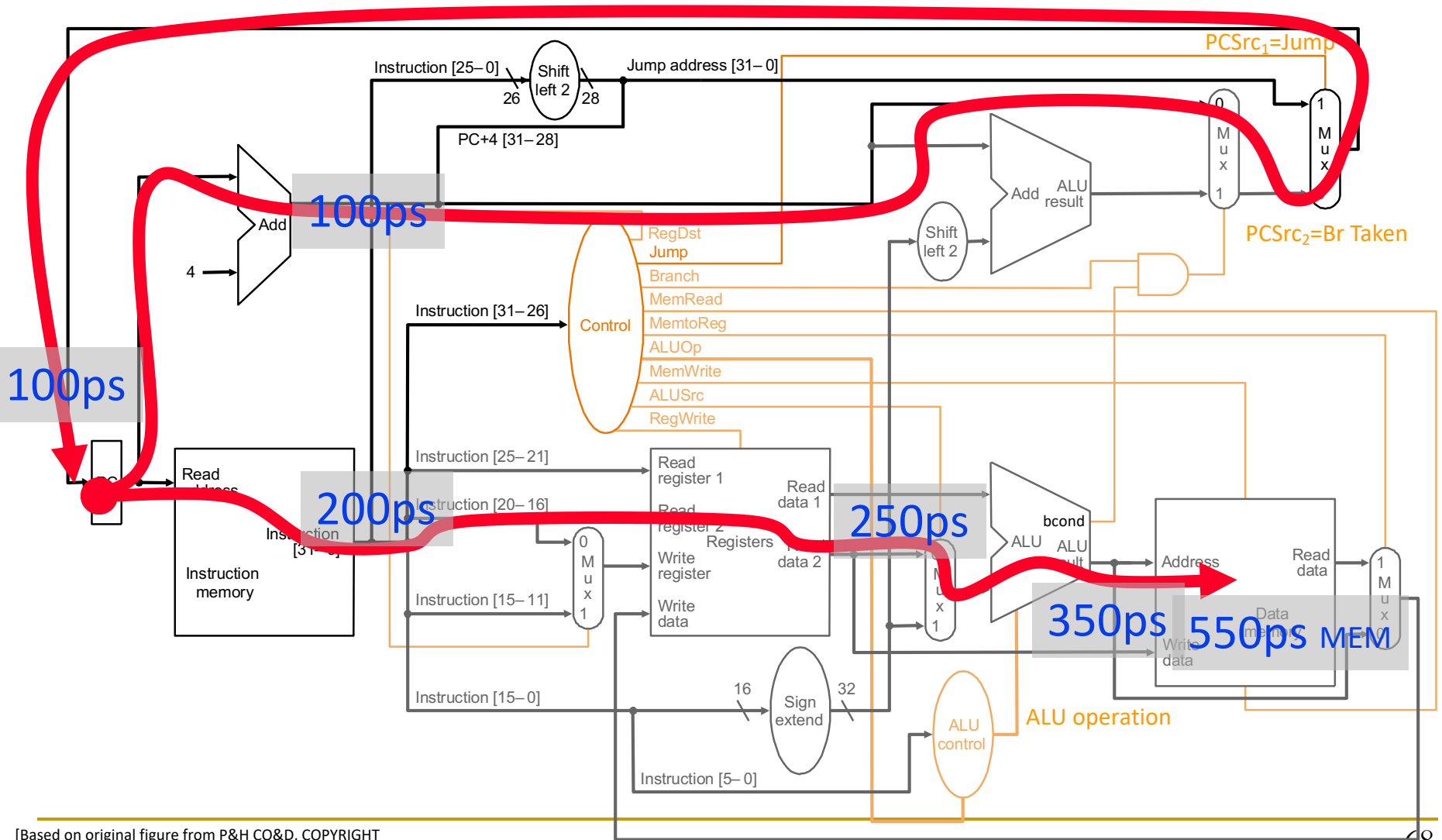


# Branch Taken

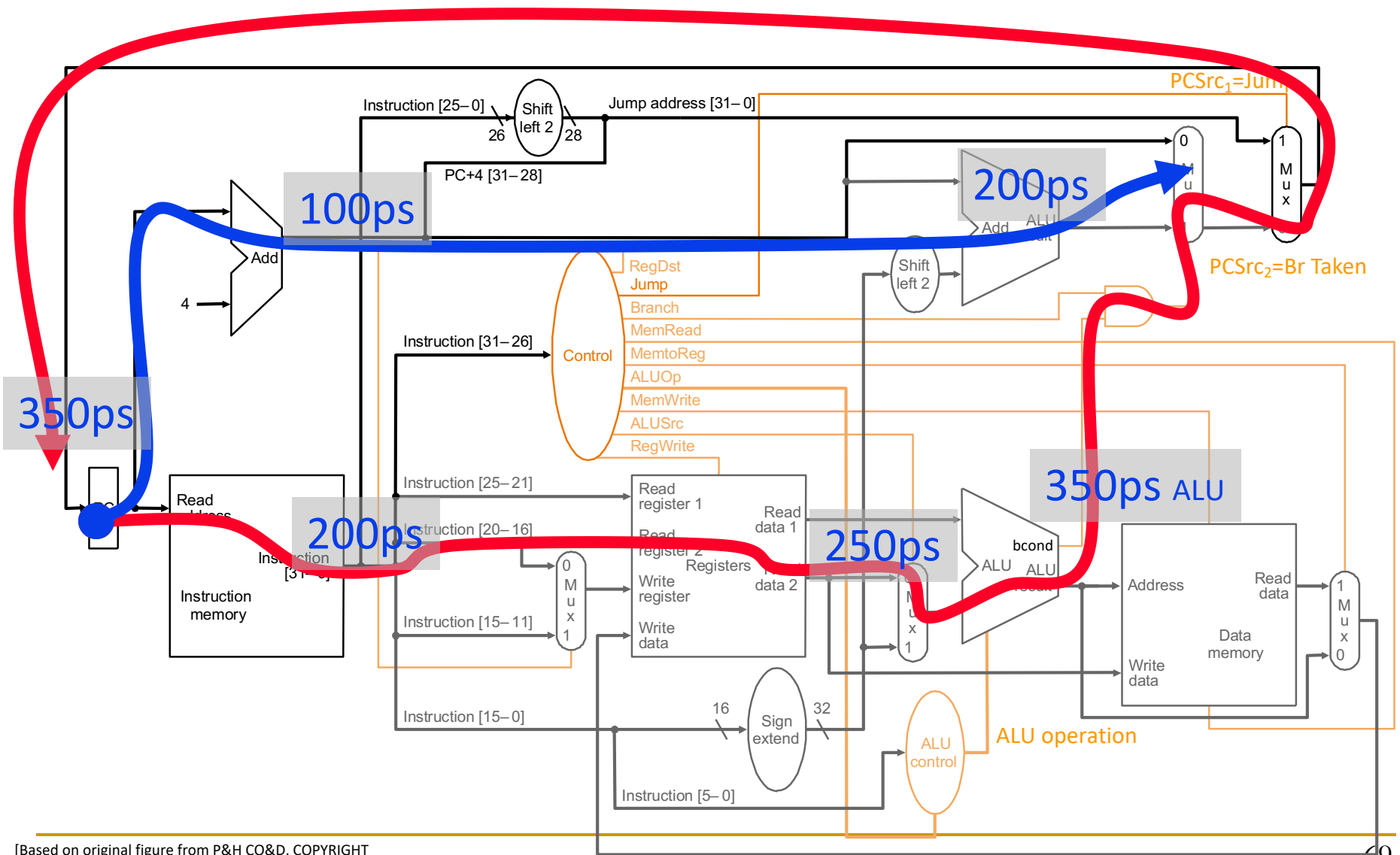

[Based on original figure from P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

# Jump

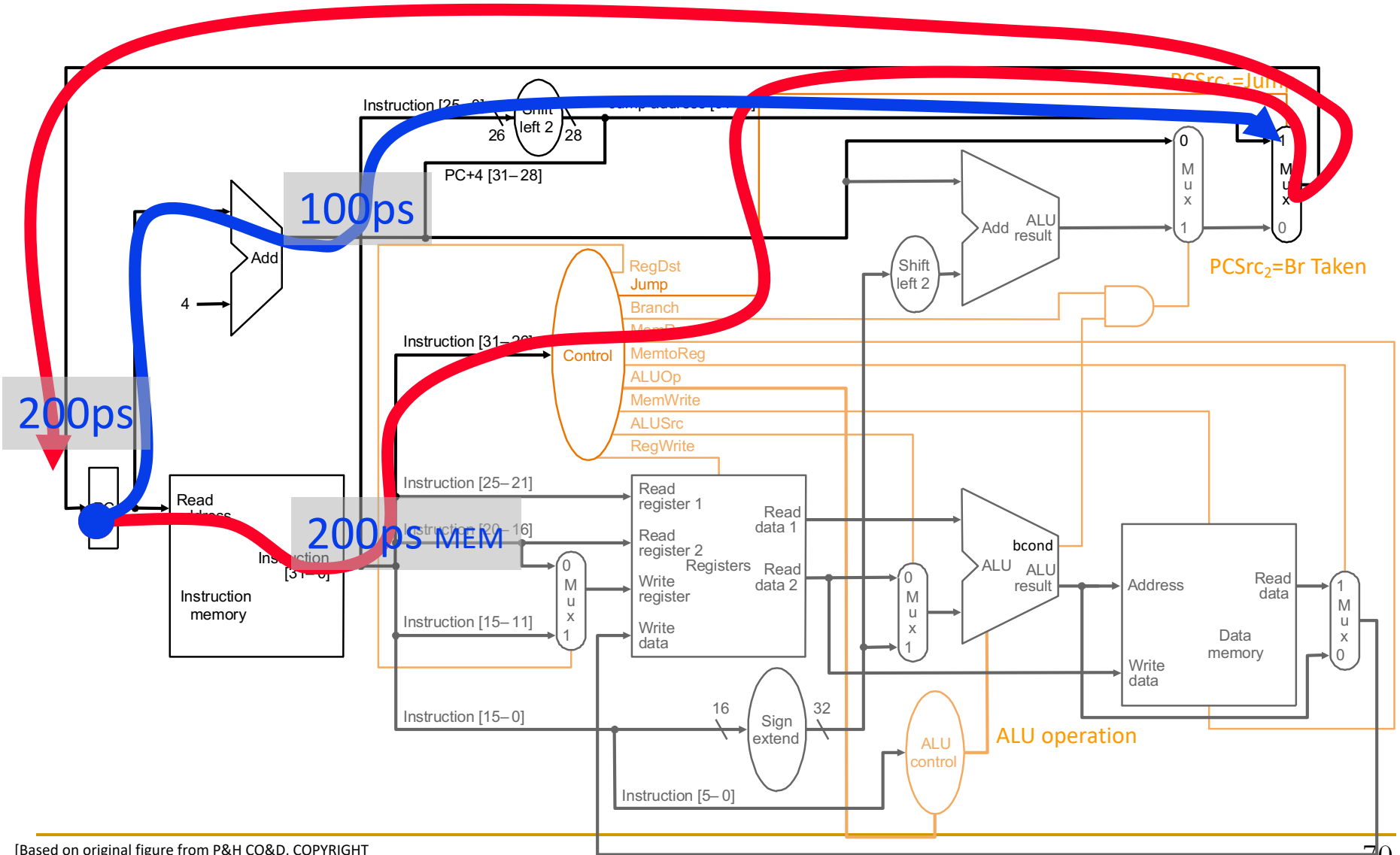

# What About Control Logic?

Like bcond

---

- How does that affect the critical path?
- Food for thought for you:
  - Can control logic be on the critical path?
  - A note on CDC 5600: control store access too long...

# What is the Slowest Instruction to Process?

---

- Memory is not magic
- What if memory *sometimes* takes 100ms to access?
- Does it make sense to have a simple register to register add or jump to take {100ms+all else to do a memory operation}?
- And, what if you need to access memory more than once to process an instruction?
  - Which instructions need this?
  - Do you provide multiple ports to memory?



# Single Cycle uArch: Complexity

---

- Contrived
  - All instructions run as slow as the slowest instruction
- Inefficient
  - All instructions run as slow as the slowest instruction
  - Must provide worst-case combinational resources in parallel as required by any instruction
  - Need to replicate a resource if it is needed more than once by an instruction during different parts of the instruction processing cycle
- Not necessarily the simplest way to implement an ISA
  - Single-cycle implementation of REP MOVS (x86) or INDEX (VAX)?
- Not easy to optimize/improve performance
  - Optimizing the common case does not work (e.g. common instructions)
  - Need to optimize the worst case all the time

# (Micro)architecture Design Principles

---

## ■ Critical path design

- Find and **decrease the maximum combinational logic delay**
- Break a path into multiple cycles if it takes too long

## ■ Bread and butter (common case) design

- **Spend time and resources on where it matters most**
  - i.e., improve what the machine is really designed to do
- Common case vs. uncommon case

## ■ Balanced design

- **Balance** instruction/data flow through hardware components
- **Design to eliminate bottlenecks:** balance the hardware for the work

# Capacitive Power dissipation

If you want to increase your frequency, you may also need to increase the voltage

Capacitance:  
Function of wire  
length, transistor size

Supply Voltage:  
Has been dropping  
with successive fab  
generations

$$\text{Power} \sim \frac{1}{2} CV^2Af$$

Activity factor:  
How often, on average,  
do wires switch?

Clock frequency:  
Increasing...

# Single-Cycle Design vs. Design Principles

---

## ■ Critical path design

- Find the maximum combinational logic delay and increase it

## ■ Bread and butter (common case) design

- Spend time and resources on where it matters
  - i.e., improve what the machine is really designed to do
- Common case vs. uncommon case
  - i.e., if you execute add most of the time

## ■ Balanced design

- Balance instruction/data flow through hardware components
- Balance the hardware needed to accomplish the work

# Aside: System Design Principles

---

- When designing computer systems/architectures, it is important to follow good principles
- Remember: “principled design” from our first lecture
  - Frank Lloyd Wright: “architecture [...] based upon **principle**, and not upon **precedent**”

# Aside: From Lecture 1

---

- “architecture [...] based upon **principle**, and not upon **precedent**”





# Aside: System Design Principles

---

- We will continue to cover key principles in this course
- Here are some references where you can learn more
- Yale Patt, "Requirements, Bottlenecks, and Good Fortune: Agents for Microprocessor Evolution," Proc. of IEEE, 2001. (Levels of transformation, design point, etc)
- Mike Flynn, "Very High-Speed Computing Systems," Proc. of IEEE, 1966. (Flynn's Bottleneck → Balanced design)
- Gene M. Amdahl, "Validity of the single processor approach to achieving large scale computing capabilities," AFIPS Conference, April 1967. (Amdahl's Law → Common-case design)
- Butler W. Lampson, "Hints for Computer System Design," ACM Operating Systems Review, 1983.
  - <http://research.microsoft.com/pubs/68221/acrobat.pdf>

# Aside: One Important Principle

---

- Keep it simple
- “Everything should be made as simple as possible, but no simpler.”
  - Albert Einstein
- And, do not forget: “An engineer is a person who can do for a dime what any fool can do for a dollar.”
- For more, see:
  - Butler W. Lampson, “[Hints for Computer System Design](#),” ACM Operating Systems Review, 1983.
  - <http://research.microsoft.com/pubs/68221/acrobat.pdf>



# Multi-Cycle Microarchitectures